

Introduction to Simulink


Eman Alashwali

Objectives


- Introduction to Simulink (MATLAB)
- Designing Digital Circuits using Simulink

Starting Matlab

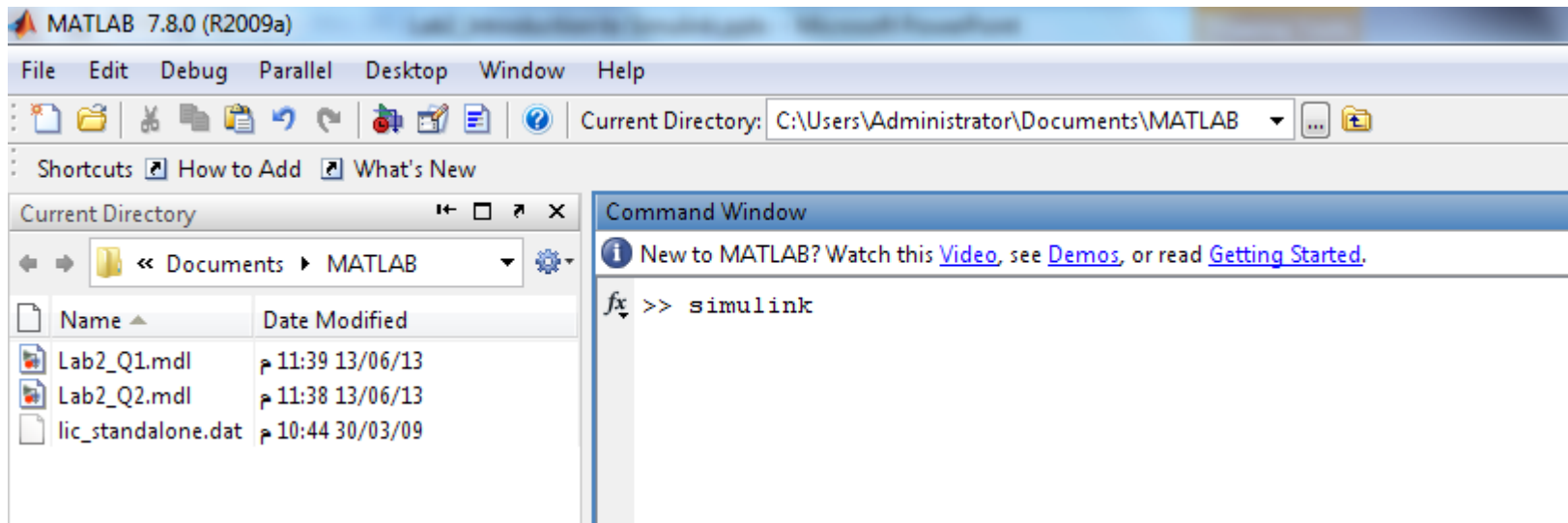
- From Start -> Matlab
- In the command line, type: `simulink` -> Press Enter and wait for a moment (it may take few seconds)




• Yo

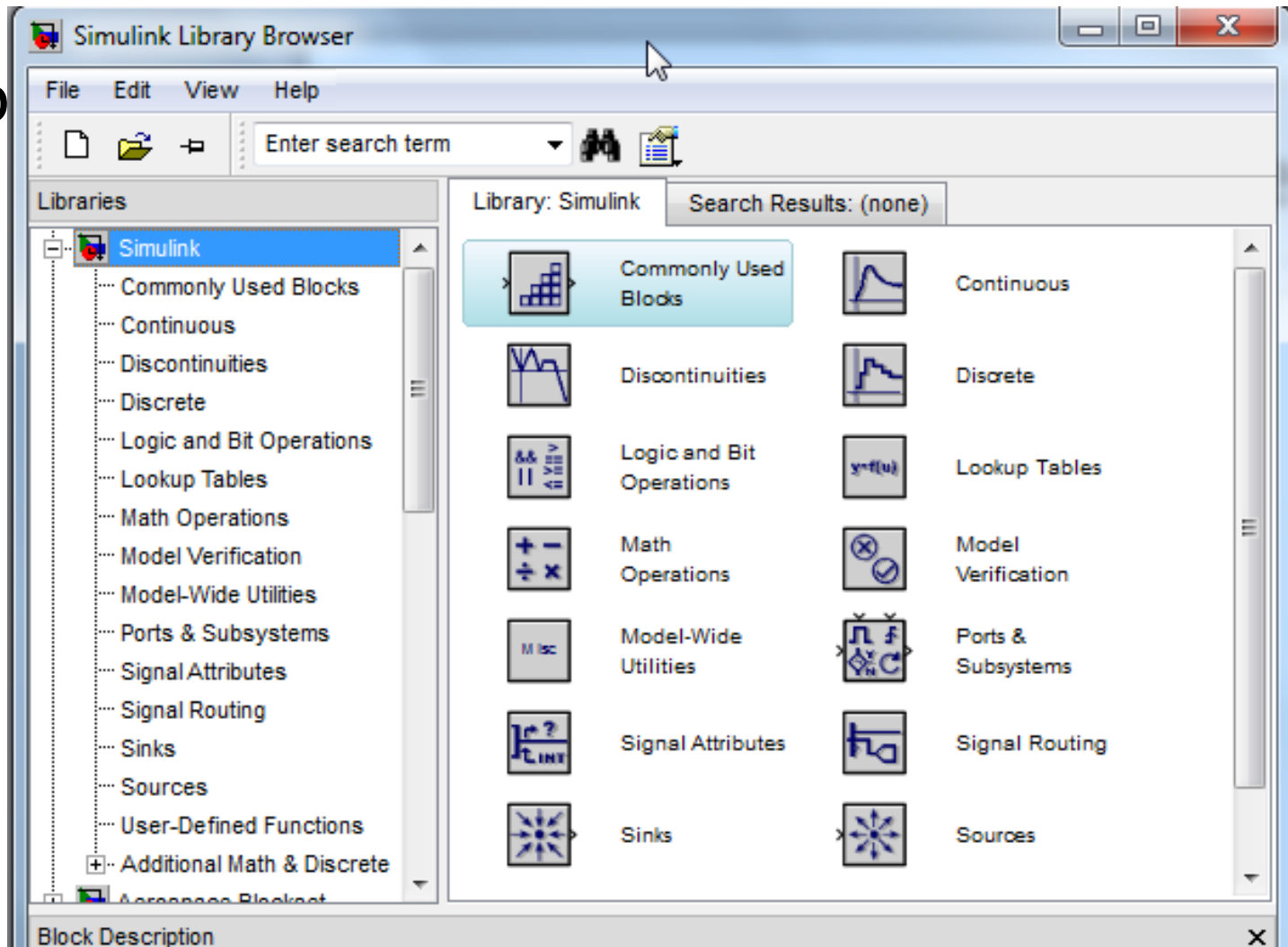

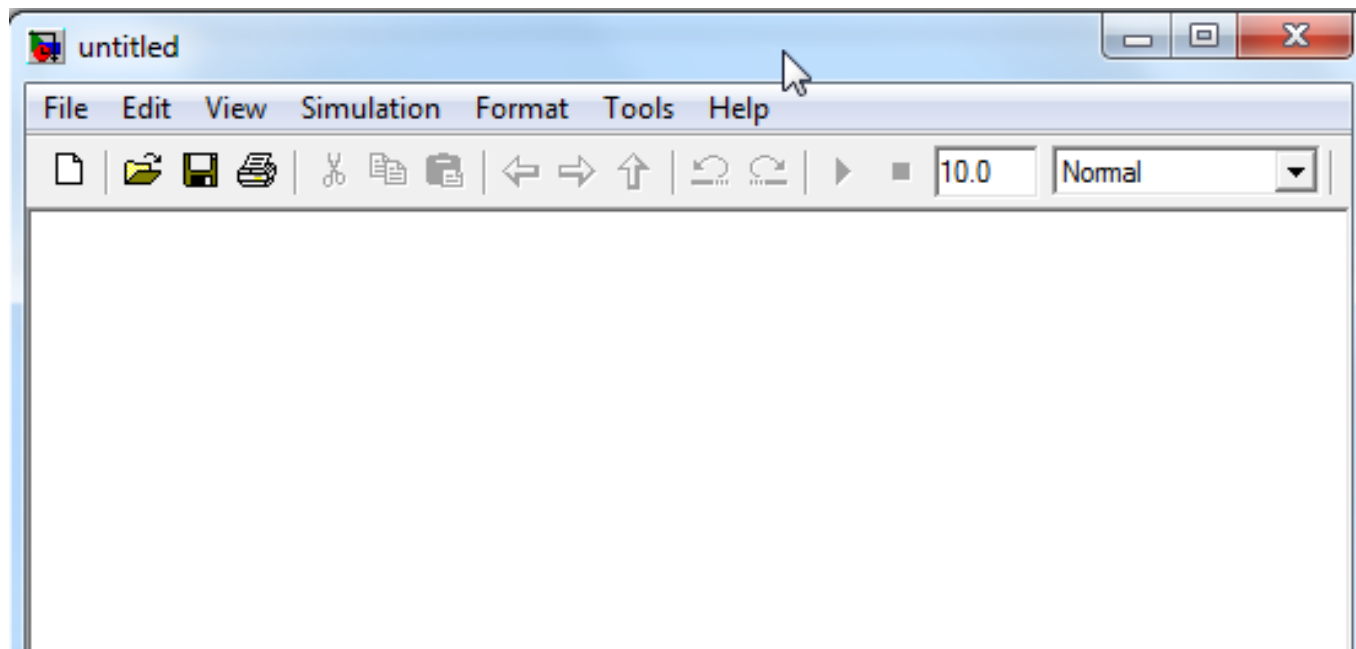
- From File -> New -> Model
- You will get a blank window like this:



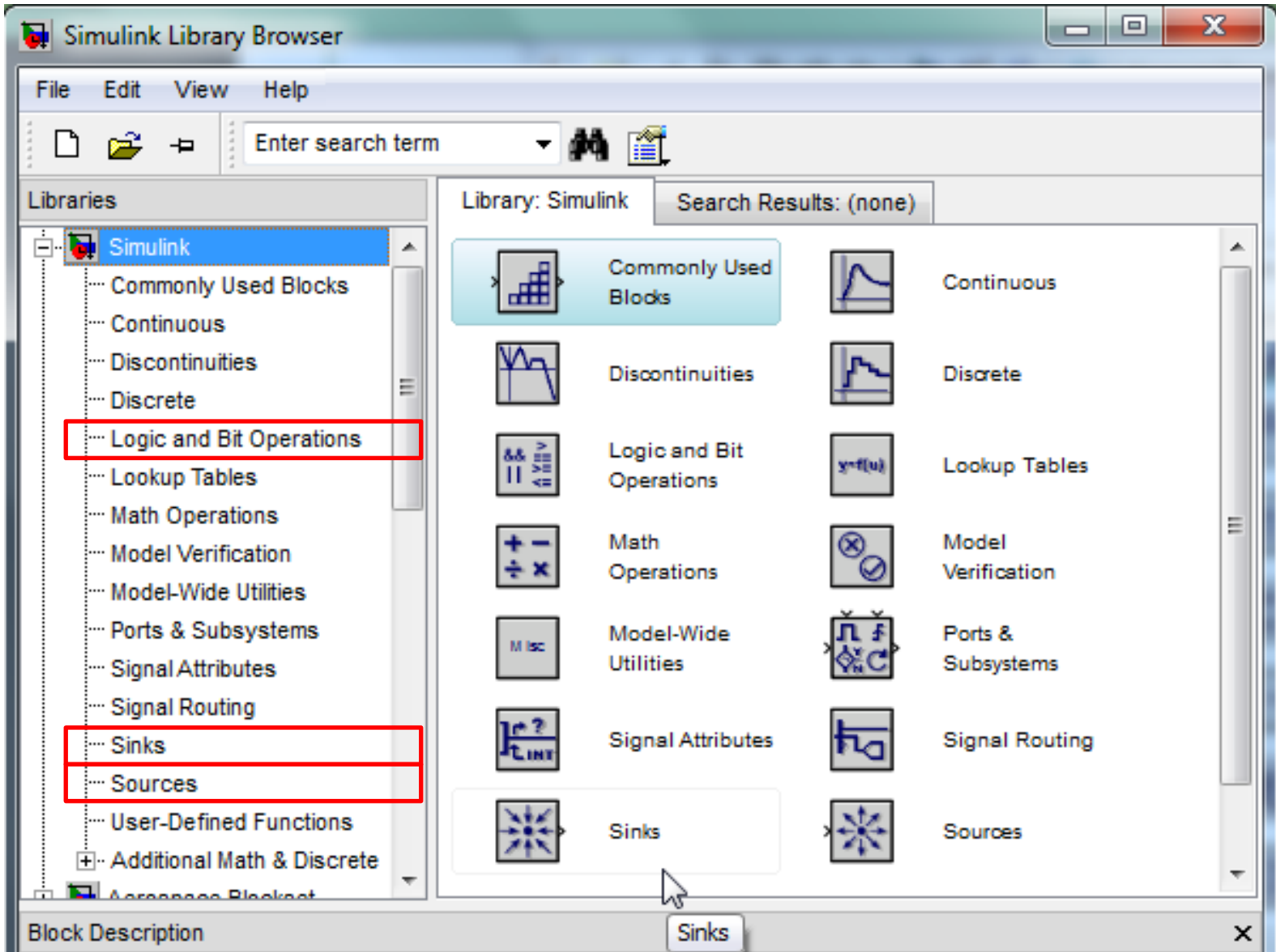
- To draw a circuit, we have 3 main categories for the components:
 - Input -> *Source*
 - Gate -> *Logical and Bit Operation*
 - Output -> *Sink*



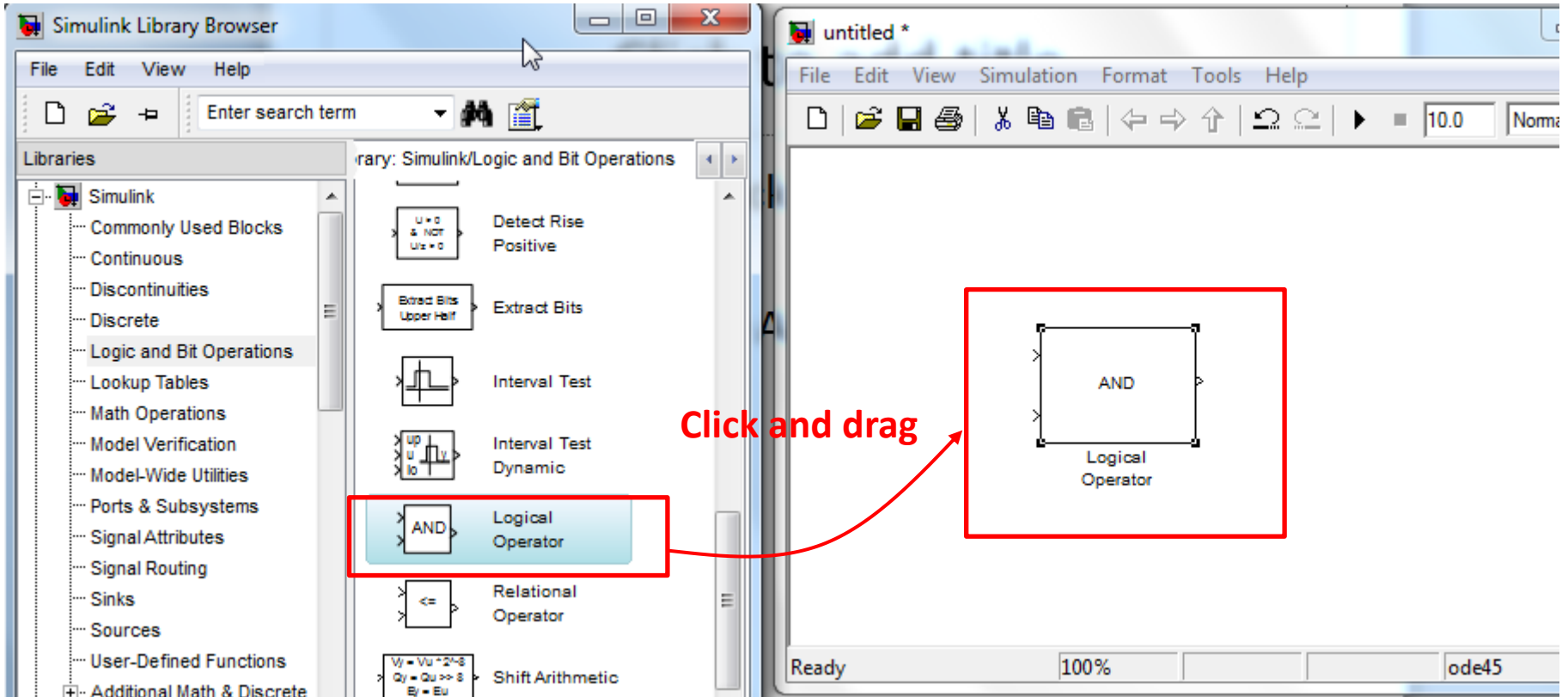
- To draw a gate, click on Logic and Bit Operations.
- Click and drag the AND logical operator



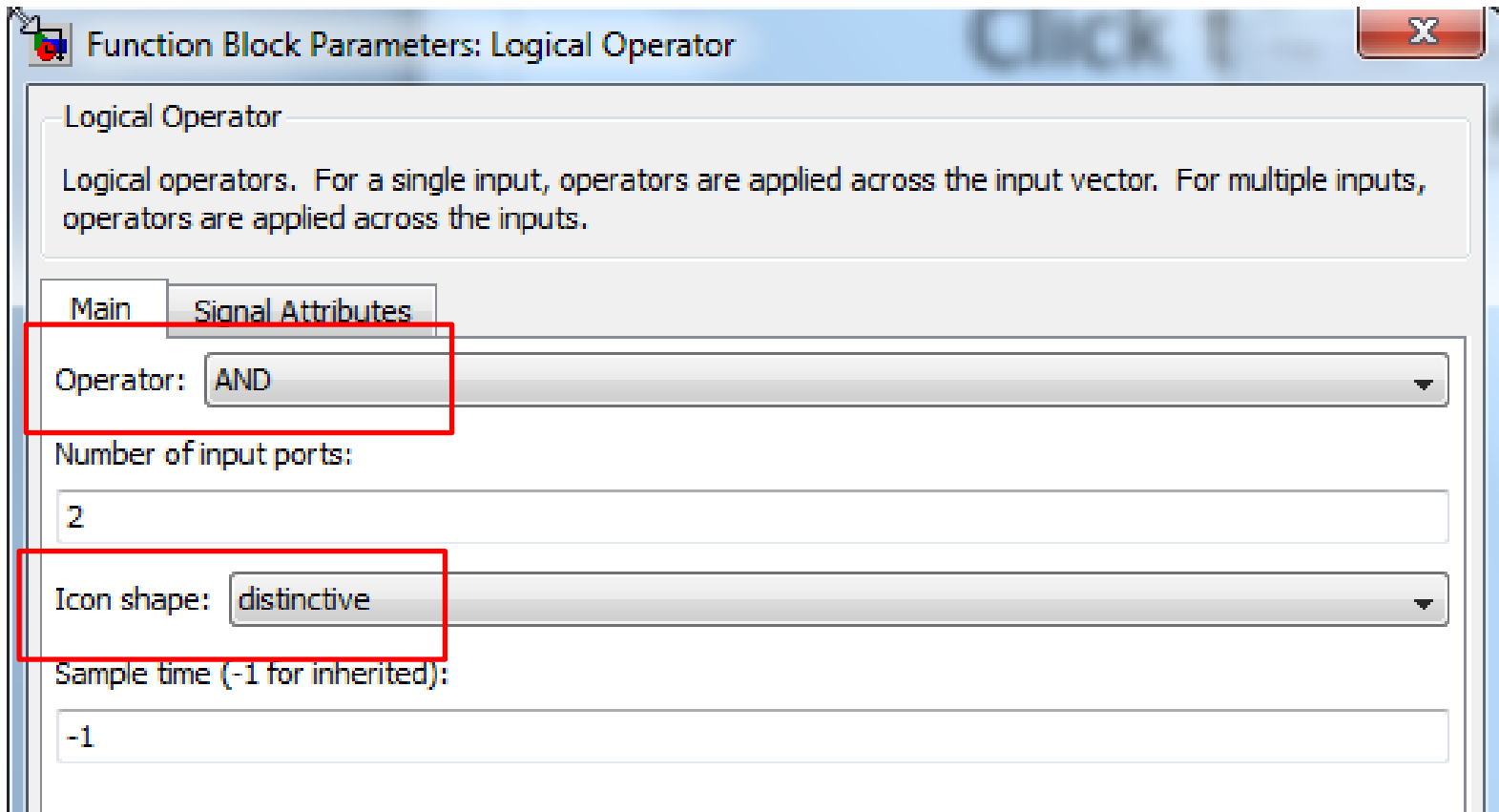- To change its shape and type (to OR, NAND, etc.) double-click on the gate
- Operator: AND / OR / NOR
- Icon shape: select distinctive to make the known shape for the gate operator




 - After changing the logical operator to AND, and the shape to distinctive, the AND gate looks like:




Logical
Operator

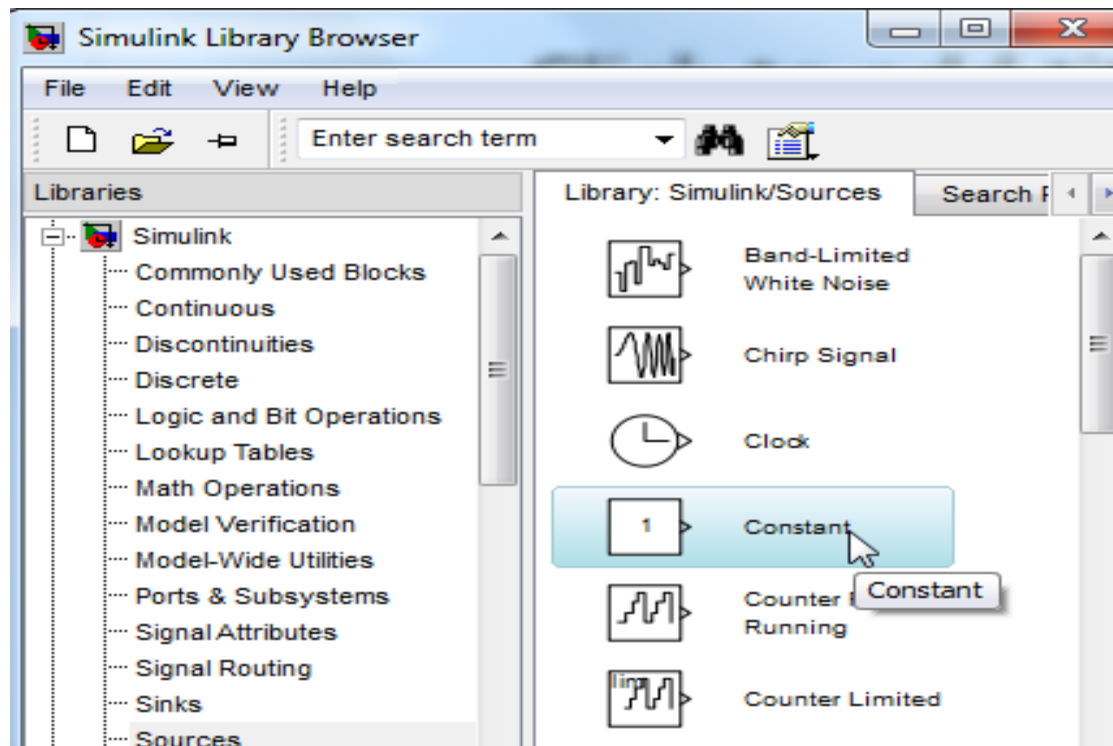
- To add a constant input, from Source -> Constant
- Drag and drop the constant rectangle



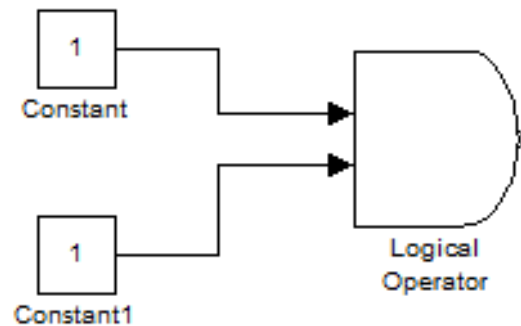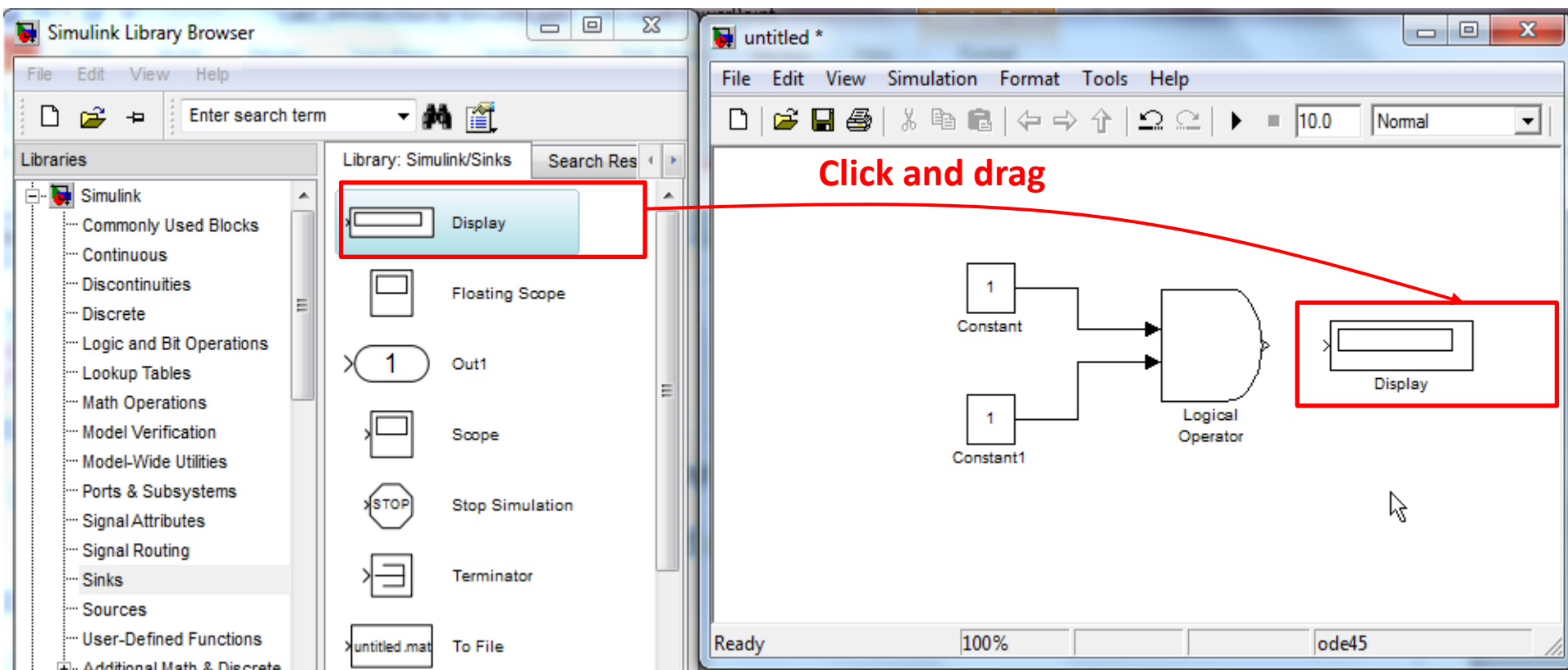
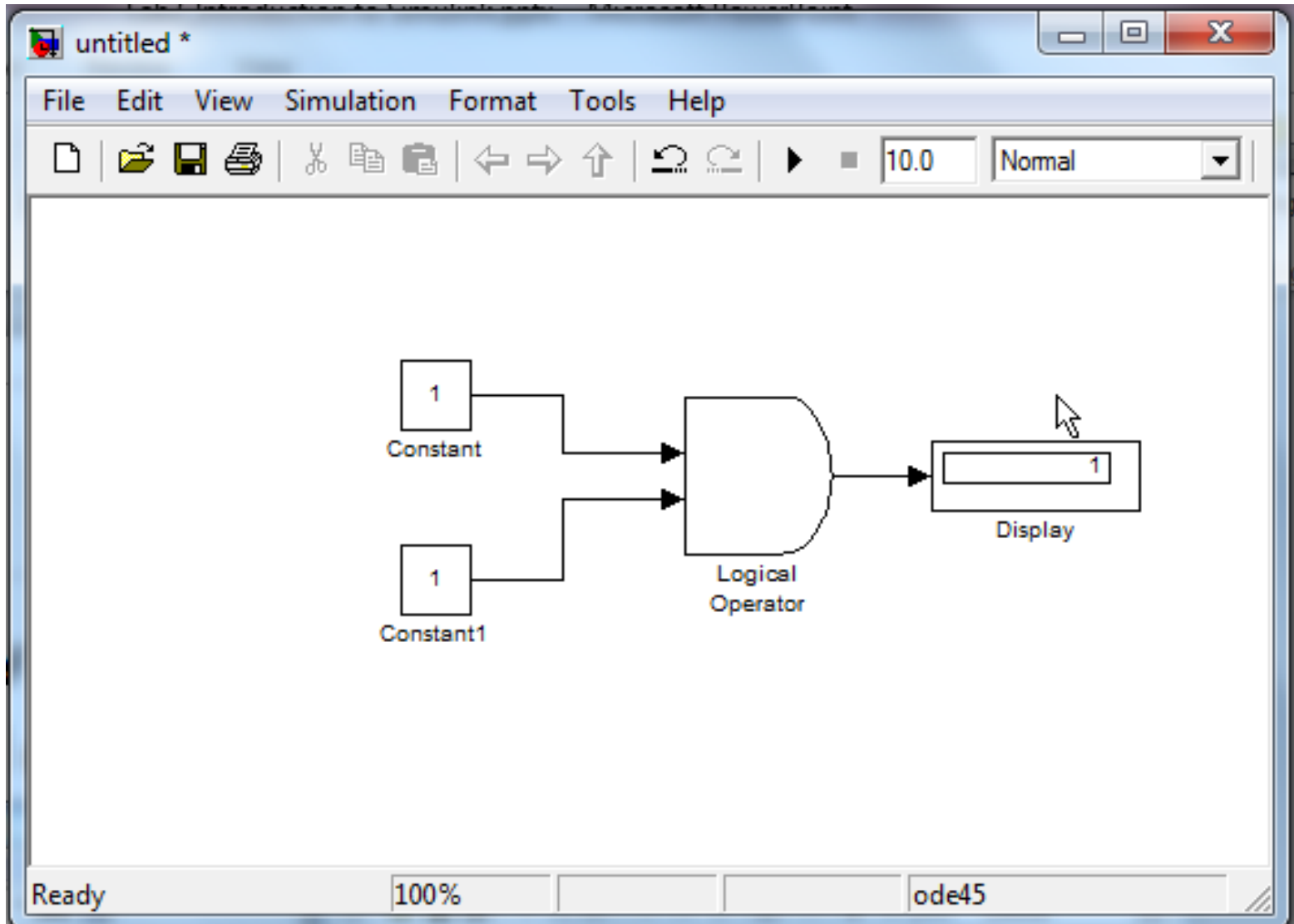
- To change the constant value, double-click on the constant rectangle
- Draw a line by clicking on the constant -> click on the constant + shift -> click on the AND gate



- To display the output, click on the Sinks
- Drag and drop a Display



- Draw a line from the AND gate to the Display rectangle
- Run your Model by click on the *Start Simulation* button A small, light gray rectangular button with a black right-pointing triangle (play icon) in the center.
- You will see the result in the Display rectangle
- Try to change the constants values and watch the Display




To Create a Subsystem


- You need to create subsystems if you have complicated circuit. It allows you to hide the small details inside a subsystem
- Select the details you want to hide -> Right click -> choose “Create subsystem from selection”

Subsystem Example

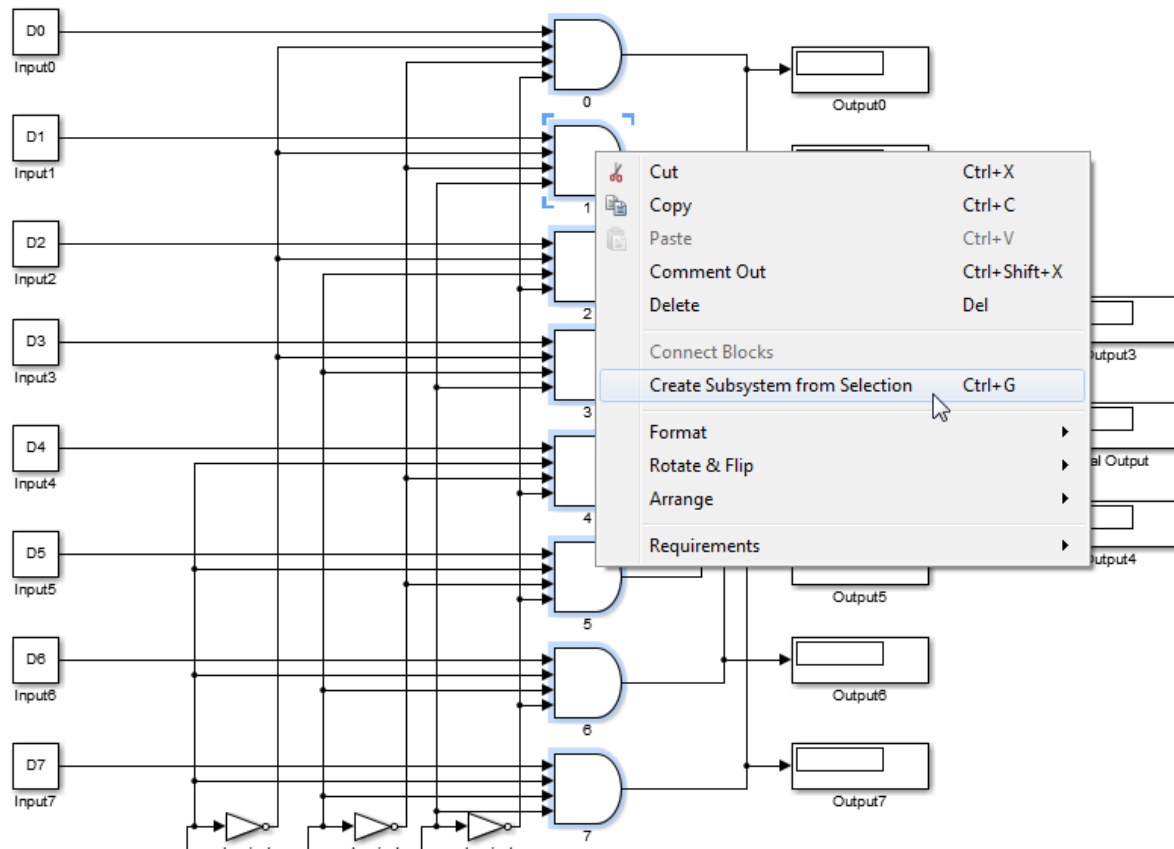- I selected all the AND gates in this Multiplexer



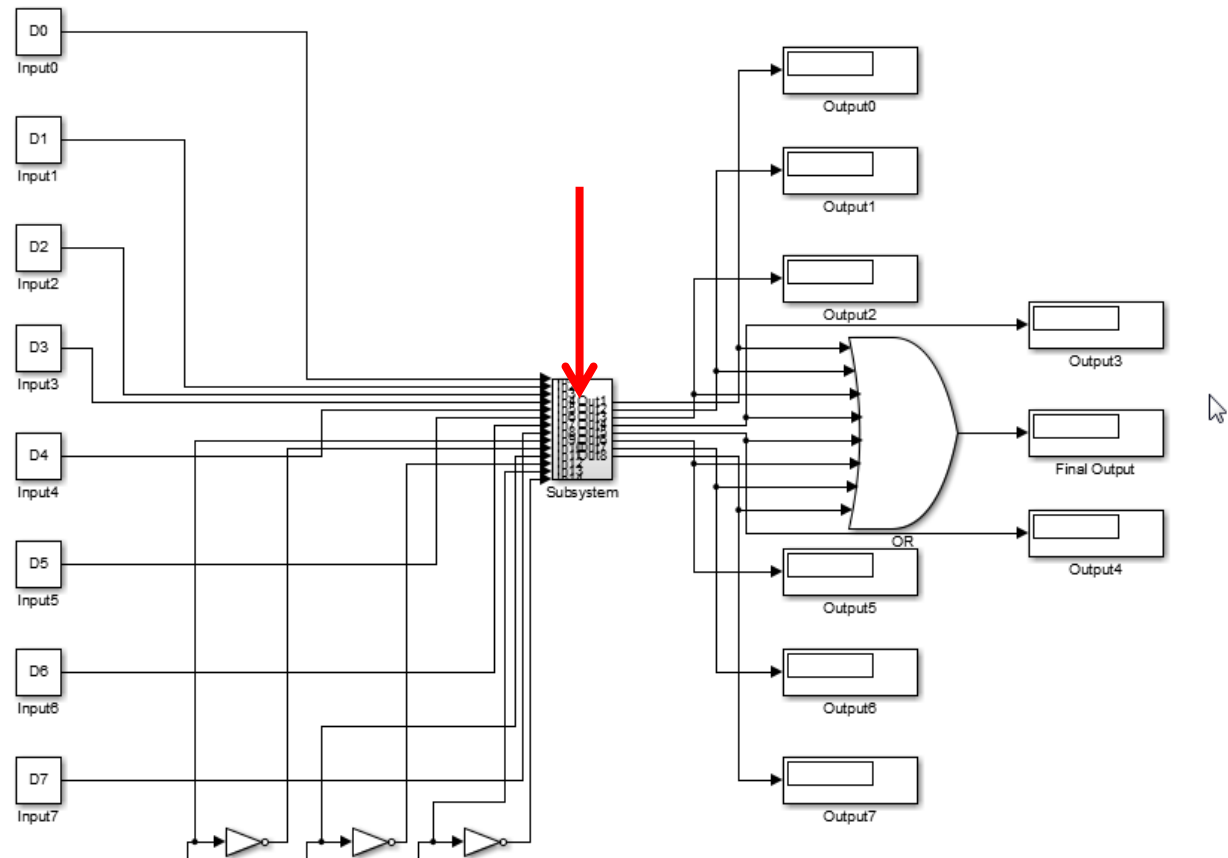- The subsystem hides all the AND gates in one component



Lab Exercise

- Draw the following two functions
 - $AB + AC$
 - $A(B+C)$
- Build the two expressions truth table
- Try to use the same constants value in the two circuits. ***What do you observe ?***

HW#1

- Install Matlab Simulink in your own machine
- The SW is available in Student copy. You can buy it online from:
https://www.mathworks.com/store/link/products/student/?s_tid=ac_buy_sv_cta
- Cost USD \$ 89
- Practice drawing circuits

References

- King Abdulaziz University, faculty of computing & IT, CPIS – 210 lab manual Computer Architecture & Organization, pages (8 &9) by Abdul Rauf Malik